

NAME: ROSHAN TAPAS BASU

R.NO: 15BCE0837

EXPEERIMENT 9: FLIP FLOPS

PART A:


AIM:

To verify the RS, D, JK and T flip flops.


TRUTH TABLE:

Q_t	A	B	S-R Q_{t+1}	J-K Q_{t+1}	D(inp:A) Q_{t+1}	T(inp:A) Q_{t+1}
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	1	1	1	1
0	1	1	IND	1	1	1
1	0	0	1	1	0	1
1	0	1	0	0	0	1
1	1	0	1	1	1	0
1	1	1	IND	0	1	0

CIRCUIT DIAGRAM:

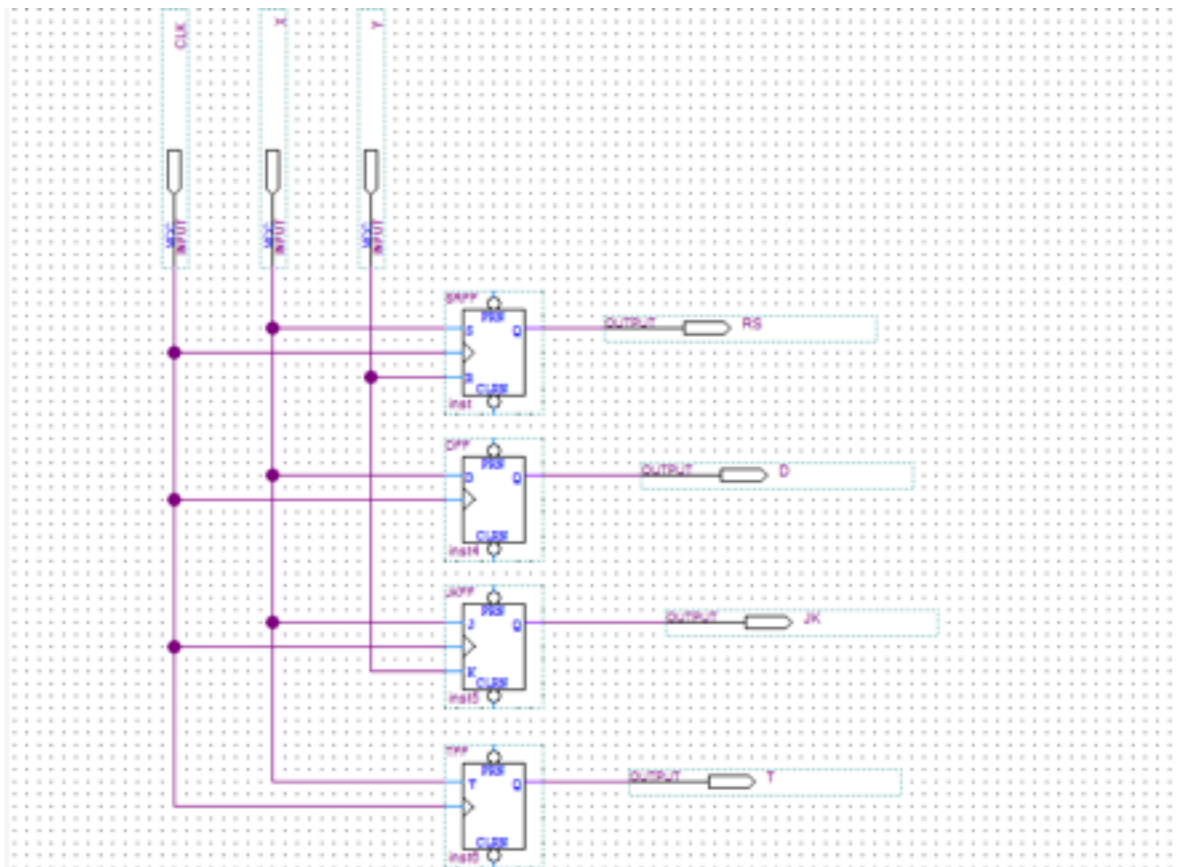

WAVEFORM:

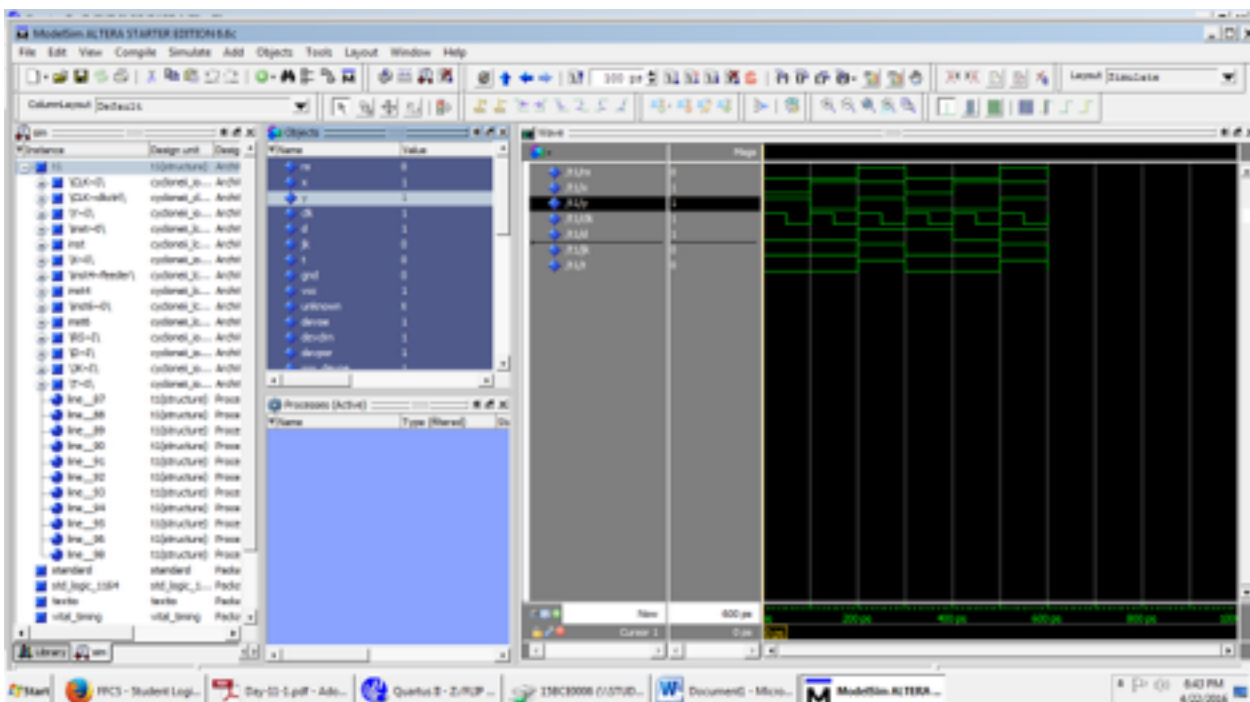

PART B:

AIM:

Design and implement three bit synchronous binary up-counter.

TRUTH TABLE:

At	Bt	Ct	At+1	Bt+1	Ct+1	TA	TB	TC
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1


EXPRESSION:

$$TA = BC$$


$$TB = C$$

$$TC = 1$$

CIRCUIT DIAGRAM:

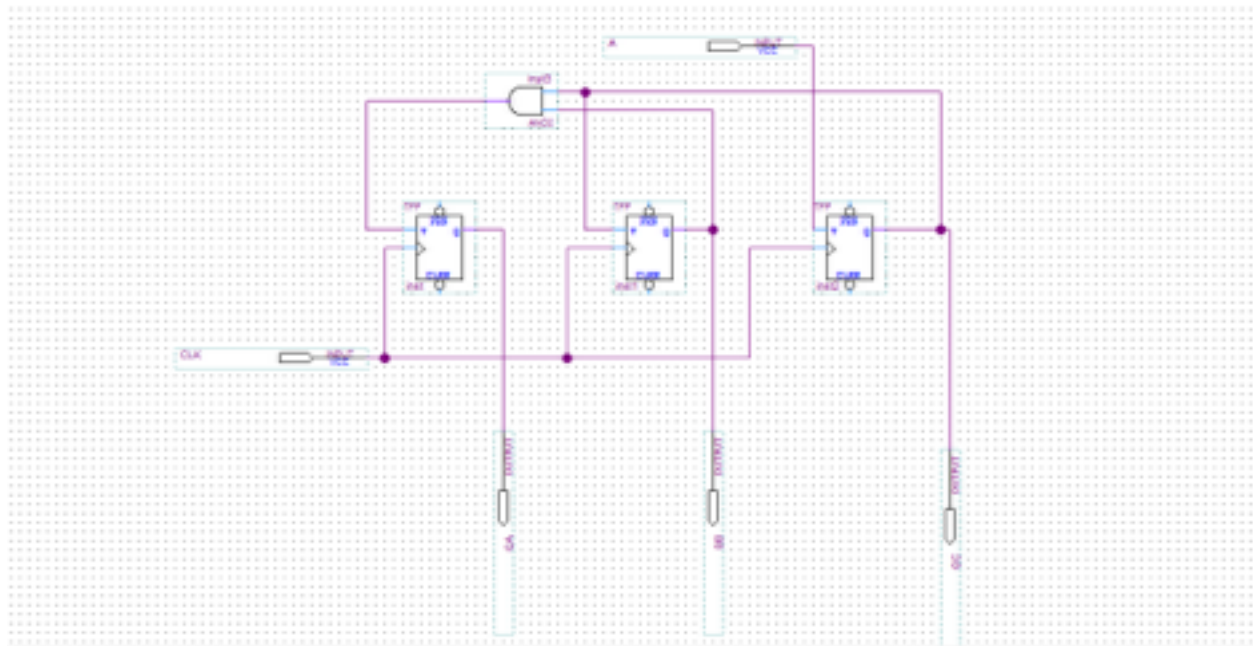

WAVEFORM:

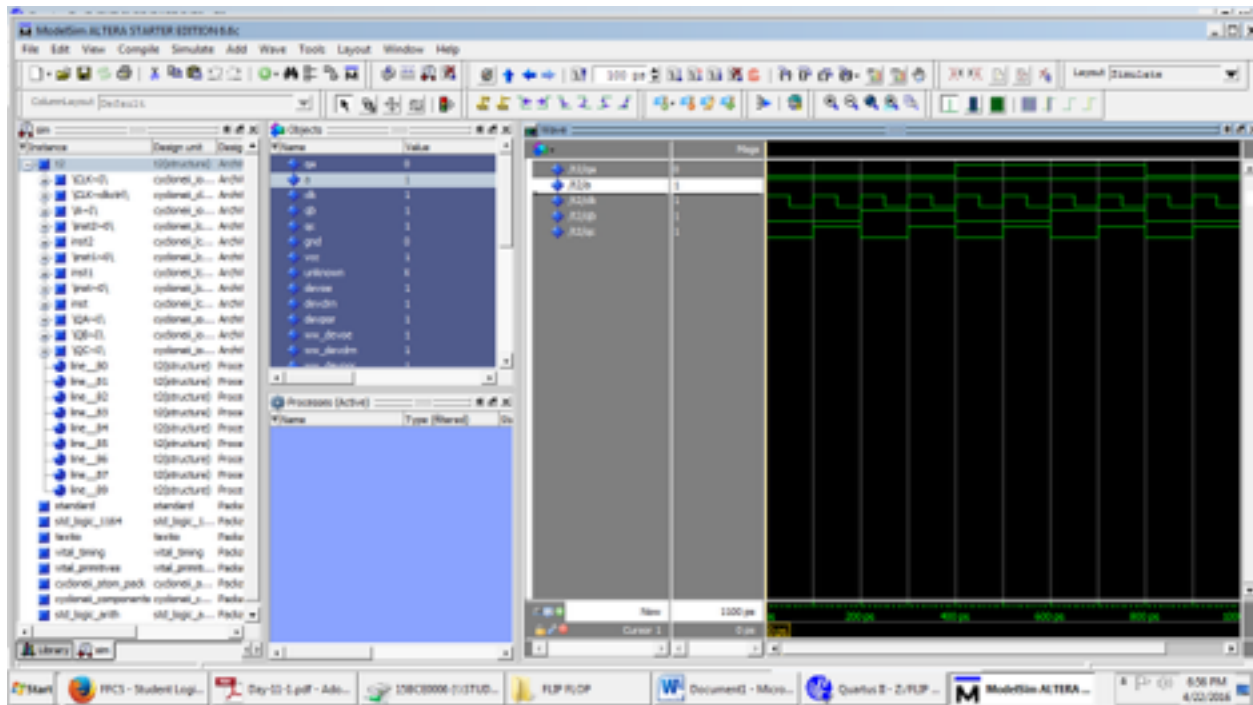

PART C:

AIM:

Design the control circuit for a vending machine with the following specifications:

- The vending machine accepts 5-rupee coin and 10-rupee coin.
- When the machine has received 10 rupees it delivers a package of candy.
- If too much money has been added, the machine returns the difference.
- Candy will not be released if sufficient money is not added.
- When the candy has been released, the release mechanism brings the circuit back to the original, starting state.

TRUTH TABLE:

X	Y	Q _t	Q _{t+1}	A	B	C	TA
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	1	0
0	1	1	0	0	1	1	1
1	0	0	1	0	0	0	1
1	0	1	0	0	0	1	1
1	1	0	0	0	1	1	0
1	1	1	0	1	0	1	1

EXPRESSION:


$$TA = YQ_t + XY'$$

$$A = XYQ_t$$

$$B = Y[X \text{ XOR } Q_t]$$

$$C = Y + XQ_t'$$

CIRCUIT DIAGRAM:

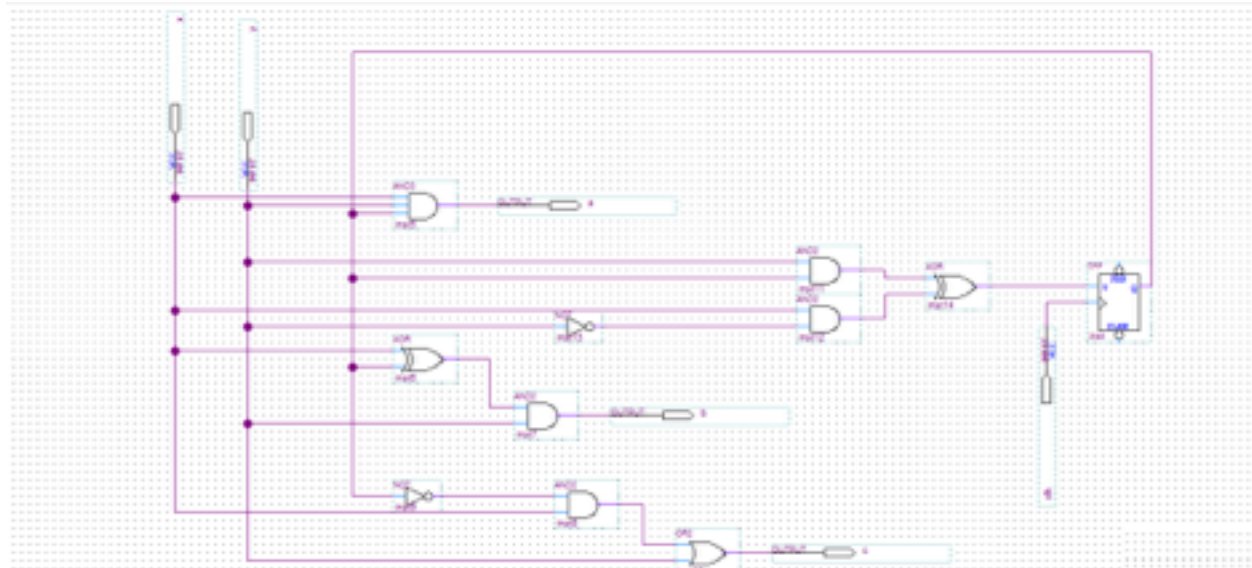

WAVEFORM:

